

Assignment

by 2023643 -

Submission date: 21-Apr-2025 06:13AM (UTC-0700)

Submission ID: 2652324234

File name: coal_project_final.pdf (1.87M)

Word count: 6304

Character count: 34972



Ghulam Ishaq Khan Institute of Engineering
Sciences and Technology

Design and Implementation of a Basic 22-bit Core Processor

Submitted To:
Mr Salman Ashraf (Course Instructor)

Submitted By:
Shafiq Hussain (2023643)
Niaz Ali (2023573)
Abdul Moeed (2023009)
Mian Muhammad Owais (2023316)

Date of Submission: April 28, 2025

COURSE: COMPUTER ORGANIZATION AND ASSEMBLY LANGUAGE
COURSE CODE: CE222
FACULTY OF COMPUTER SCIENCE (FCSE)

Acknowledgements

The authors of this report would like to acknowledge the hard work and dedication of the entire team. Each member contributed significantly towards the design, development, and documentation of this project. Through their consistent efforts and collaboration, the team was able to tackle complex concepts and transform them into a functional and efficient computer organizational model. The journey was both challenging and rewarding, and the success of this project stands as a testament to the team's commitment and teamwork.

Table of Contents

Acknowledgements	2
1. Abstract	5
2. Theory and Design	5
2.1 Objectives	5
2.2 Theoretical Background:	6
2.2.1 Noteworthy Assumptions	6
2.3 Definition of the BUS Network	7
2.4 Arithmetic Logic & Shift Unit (ALU).....	8
2.4.1 Arithmetic Microoperations	8
2.4.2 Logic Microoperations	12
2.4.3 Shift Microoperations	13
2.4.4 Miscellaneous Circuit Units for New Microoperations.....	15
2.4.5 Complete ALU Design.....	16
2.5 Register Selection and Main Memory Organization	18
2.5.1 Register Organization	18
2.6 Instruction Format	19
2.7 The Common Integrator	20
3. Definition & Implementation of the Instruction Set	21
3.1 The Control Unit	22
3.3 Fetch-Decode Cycle	25
3.2 Input/Output and Interrupt Handling	25
4. Complete Computer Description	27
5. C++ Simulator	29
Appendix	30
A. Decoder	30
B. Three State Gate	30
C. Multiplexer	31
D. Half Adder	31
E. Full Adder	31
Bibliography	32

Figure Listings

Figure 1: Four Operational Attributes of BACE	5
Figure 2: General Purpose von Neumann Architecture	6
Figure 3: Bus Structure using Decoder	7
Figure 4: Bus Structure using a single quad-multiplexer	8
Figure 5: Bus structure using cascaded quad-multiplexer	8
Figure 6: Adder-Subtractor Circuit with Look-Ahead Logic	9
Figure 7: Look-Ahead Logic Circuit Internal Working	10
Figure 8: Arithmetic Circuit	11
Figure 9: Logic Unit	12
Figure 10: Shift Microoperations	13
Figure 11: Barrel Shifter Circuits	13~15
Figure 12: Code Converters	15
Figure 13: Comparators	16
Figure 14: Complete ALU	16
Figure 15: Common Integrator	20
Figure 16: Control Unit	23
Figure 17: Sequencer and Decoder Combination Waveform	23
Figure 18: Sequencer and Decoder Combination Truth Table	24
Figure 19: Fetch-Decode Cycle for all instructions	25
Figure 20: Input/Output Handling Flowcharts	26

1. Abstract

In this report, the designing process imparted to us in the course CE222-Computer Organization and Assembly Language is followed insofar as to construct the logical foundations of a structurally sound and functional Central Processing Unit (CPU) followed by the complete instruction set definition. The report follows the chronological steps of: designing the bus structure, ALU, and CU; selecting the necessary and appropriate registers and memory configurations; defining the instruction set and format of the B22Core processor from a repertoire of options and customizations. Each section details the purpose and theoretical background behind each component whilst also keeping in view the organizational aspect through extensive use of block diagrams and flowcharts. Moreover, the new additions made in the B22Core processor as compared to the original Basic Computer have been detailed and justified for their inclusion and need, and as required, their working has been further elaborated through subsections dedicated to explaining their functionality. The crux of the report is the enhanced ALU and increased number of instructions in the instruction set. Lastly, the representations of the computer microoperations in the Complete Computer Description were facilitated through the use of Register Transfer Language (RTL).

2. Theory and Design

2.1 Objectives

To the ends of implementing a logical CPU design with exhaustive operational capabilities, the four main features of any digital computer system as enlisted below and encapsulated in Fig. 1:

- Data Transfer and Communication
- Short-Term and Long-Term Data Storage
- Data Processing
- Data Control Function

For a complete computer description, the design process has incorporated manifold functionality by taking inspiration from the Basic Computer such as a completely redesigned processor with enhanced arithmetic & logic operations, register organization, bus structure and input/output procedures. To facilitate data movement, the logical design of the bus has been elaborated with multiple addressing modes. For the purpose of storage, processor registers and main memory has been defined appropriately. Data processing has been defined through the description of a complete Instruction Set Architecture and achieved through the ALU; moreover, to accommodate and control all such requirements of the B22Core processor, an original Control Unit has been implemented.


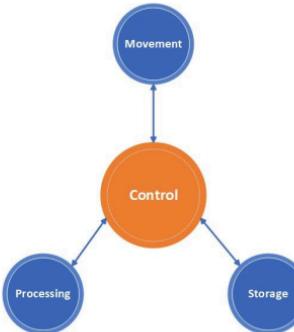


Figure 1-Four Operational Attributes of BACE

2.2 Theoretical Background:

In this section, some prerequisite concepts pertaining to the design of the B22Core processor are uncovered. In essence, the B22Core processor among numerous other processors realizes the use of the general-purpose Von Neumann Architecture as portrayed in Fig. 2. Although the Harvard Architecture is well-known for its unique features such as a separation in storage and movement between data and instructions unlike the von Neumann architecture which relies on stored program computers (i.e. data and instructions stored in the same memory medium), the latter was preferred owing to its simplicity in designing, modeling and implementation.

Figure 2-General Purpose von Neumann Architecture

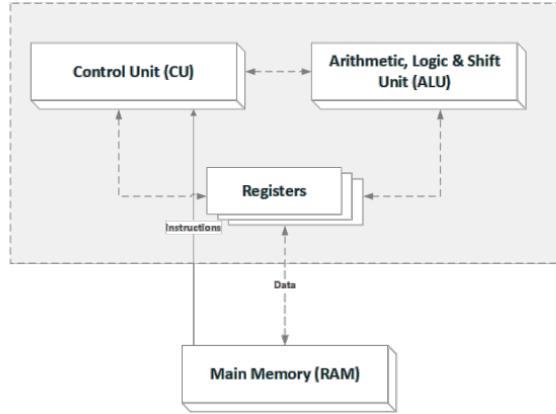

The remainder of the report will follow a top-down approach and dissect the internal workings of each of these four components, namely the Arithmetic Logic & Shift Unit (ALU), Control Unit (CU), and the manifold registers to be used by the aforementioned two units for the purpose of data processing and short-term storage. By the same token, the size and overall configuration of the main memory must also be defined for the purpose of long-term data and instructions storage.

2.2.1 Noteworthy Assumptions

Before proceeding, it is imperative to note some of the assumptions that have been made during the fabrication of this report. Firstly, if a transfer of data between two registers is shown by an RTL statement $A \leftarrow B$ where 'A' and 'B' are registers, it is assumed for all such cases that the necessary intermediate data bus connections have already been established and have not been mentioned explicitly. Moreover, it must also be noted that all such statements succeeding in the report assume parallel load capacity of the registers. As for the clock signal, it is assumed that the microoperations are executed under one clock pulse and are positive-edge triggered.

2.3 Definition of the BUS Network

Due to the immense hardware and computational overhead caused by a communication system in which each register connects to every other register, requiring $n(n-1)$ total wire connections internally, it was construed to design the overall structure of a common bus system that would centralize majority of the transfer of data that occurs in the B22Core processor from any source to all possible destinations.

The B22Core processor makes use of decoders to implement the bus system and combines the use of three-state gates, both of which are briefly elaborated below. Unlike the Basic Computer and its implementation of bus structure, our communication system has managed to reduce the amount of hardware required for implementing the same functionality.

The Basic Computer incorporated the use of 'n' decoders for n-bit registers and $\log_2 m \text{ by } m$ was the size of each decoder for 'm' registers. Furthermore, each decoder output was connected to three-state gates in order to ensure only one bit of the corresponding register was selected and passed onto the bus system by the decoder at any given time. On the other hand, the B22Core processor decreases the number of decoders required to one, which has the dimensions same $\log_2 m \text{ by } m$ but the three-state gates now connect to every bit of the registers directly as shown in Fig. 3.

By using a decoder with same number of output enable pins as number of registers and attaching the three-state gates with the registers instead of the decoder, a slight reorganization eliminated the need of multiple decoders in one bus connection. The internal working of the decoder and three-state gate as well as their truth table are given in Appendices A and B respectively.

An alternative implementation using multiplexers was also considered as shown in Fig. 4. For a sample system of 4 registers with 4-bits each, we considered using a quad multiplexer with $\log_2 8 = 3$ select lines and 4 separate quad-inputs; the benefit of this structure was that it only required one 4by1 quad multiplexer but it was quickly realized implementing a single MUX to multiplex all registers in B22Core processor would make the multiplexer circuit comparatively too large. An alternative structure is shown in Fig. 5.


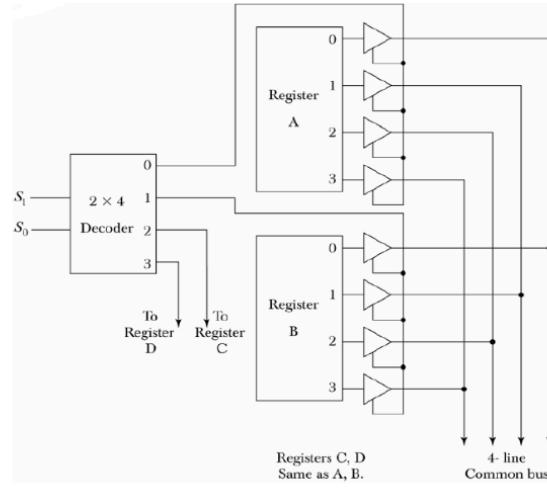


Figure 3-Bus Structure using Decoder

It must be noted that in Fig. 3, Fig. 4 and Fig. 5, the actual sizes of the registers in B22Core processor were not used and instead assumed to be 4-bits each for the sake of simplification. In the succeeding sections, such characteristics are defined exhaustively. For the information of the reader, it is mentioned beforehand that address registers typically have smaller sizes than data storing registers, and thus a default binary value of 0 was passed into each input pin of the decoder and multiplexer starting from the most significant bit which were not included in the size of the address registers but were present in the bus.

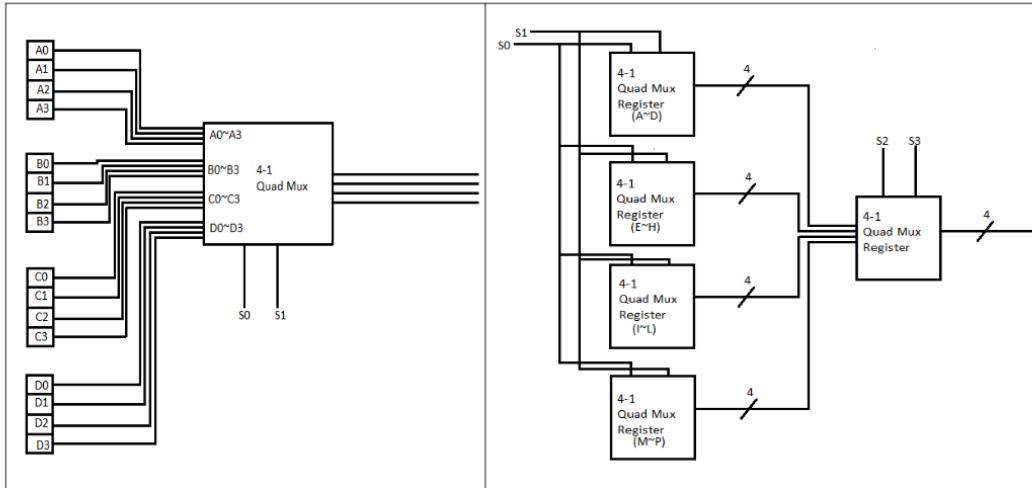

2.4 Arithmetic Logic & Shift Unit (ALU)

This section continues and completes the discussion on all the types of microoperations that can be performed by the hardwired components of the B22Core processor, namely the transfer, arithmetic, logical, and shift microoperations. The previous sections covered the transfer microoperations by defining the bus interconnections. The remaining three categories will be implemented entirely by the Arithmetic Logic & Shift Unit (i.e. ALU).

2.4.1 Arithmetic Microoperations


In this section, the most basic arithmetic microoperations performed by the ALU are summarized, followed by a discussion on a single composite arithmetic circuit that hardwires all such implementation into one unit.

The B22Core processor implements the typical arithmetic operations such as increment, decrement, addition and subtraction through the use of full-adders. Fig. 6 shows the adder-subtractor circuit alongside its truth table whereas Fig. 7 portrays the look-ahead logic. Full-adder can be derived from the connection of two half-adders. In other words, the increment operation, which would

usually be performed by the cascading of as many half-adders as the number of bits in each register, can also be performed by full-adders if appropriate configuration is achieved. Therefore there are no standalone half-adder circuits in the B22Core processor.

The full-adder circuit was designed to create the adder-subtractor circuit to decrease the number of components required to create a binary subtractor independently from the binary adder. Depending on value of Cin, addition or subtraction is performed (if cin is 0, normal addition and if it's 1, the two's complement is applied on the addend input for subtraction. Furthermore, as an extension of the adder-subtractor used in the Basic Computer, the B22Core processor counterpart also contains a look-ahead circuit in conjunction. This enables the arithmetic calculations to be done in parallel through carry generation and propagation instead of the carry rippling through each full-adder to the next sequentially in a cascaded manner, making the execution time of the B22Core processor's adder-subtractor more efficient.

Figure 6-Adder-Subtractor Circuit with Look-Ahead Logic

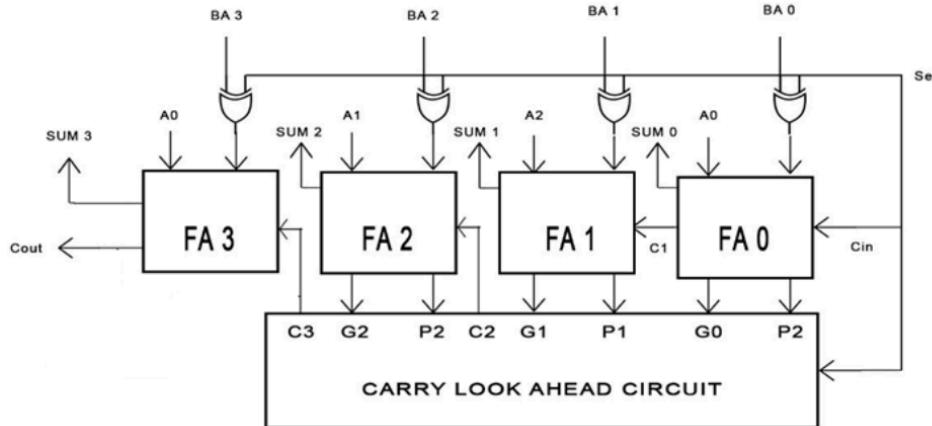

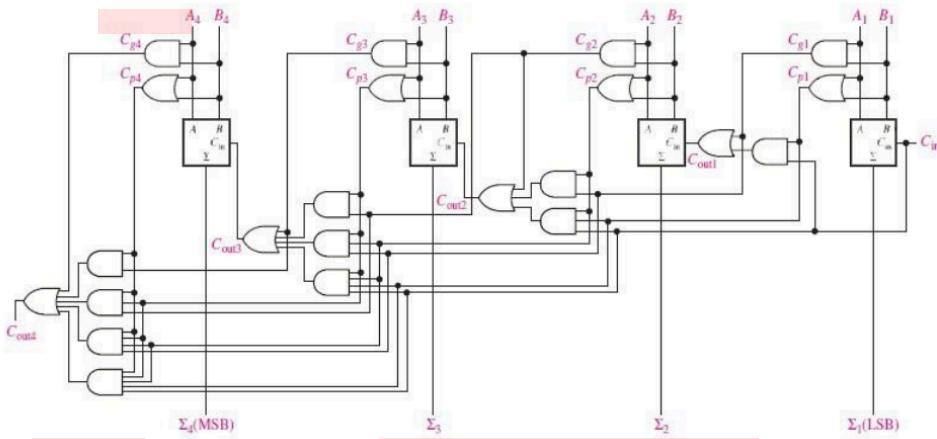


Figure 7- Look-Ahead Logic Circuit Internal Working

Full-adder 1:

$$Cout_1 = Cg_1 + Cp_1 Cin_1$$

Full-adder 2:

$$Cin_2 = Cout_1$$

$$\begin{aligned} Cout_2 &= Cg_2 + Cp_2 Cin_2 = Cg_2 + Cp_2 Cout_1 = Cg_2 + Cp_2(Cg_1 + Cp_1 Cin_1) \\ &= Cg_2 + Cp_2 Cg_1 + Cp_2 Cp_1 Cin_1 \end{aligned}$$

Full-adder 3:

$$Cin_3 = Cout_2$$

$$\begin{aligned} Cout_3 &= Cg_3 + Cp_3 Cin_3 = Cg_3 + Cp_3 Cout_2 = Cg_3 + Cp_3(Cg_2 + Cp_2 Cg_1 + Cp_2 Cp_1 Cin_1) \\ &= Cg_3 + Cp_3 Cg_2 + Cp_3 Cp_2 Cg_1 + Cp_3 Cp_2 Cp_1 Cin_1 \end{aligned}$$

Full-adder 4:

$$Cin_4 = Cout_3$$

$$Cout_4 = Cg_4 + Cp_4 Cin_4 = Cg_4 + Cp_4 Cout_3$$

$$= Cg_4 + Cp_4(Cg_3 + Cp_3 Cg_2 + Cp_3 Cp_2 Cg_1 + Cp_3 Cp_2 Cp_1 Cin_1)$$

$$= Cg_4 + Cp_4 Cg_3 + Cp_4 Cp_3 Cg_2 + Cp_4 Cp_3 Cp_2 Cg_1 + Cp_4 Cp_3 Cp_2 Cp_1 Cin_1$$

Overall, maximum functionality can be achieved from the look-ahead adder-subtractor circuit by using a modified composite arithmetic circuit as shown in Fig. 8.

The table below encapsulates the overall working of the circuit. Although eight total microoperations can be executed, the transfer procedure is repeated twice, and thus there are seven distinct microoperations that can be performed by the arithmetic circuit.

Selection			Selected Input	Output = A + Selected Input + Cin	Microoperation
S ₁	S ₀	Cin			
0	0	0	B	D = A + B	Addition
0	0	1	B	D = A + B + 1	Increment and addition
0	1	0	B'	D = A + B'	Subtraction with borrow
0	1	1	B'	D = A + B' + 1	Subtraction
1	0	0	0	D = A	Transfer A
1	0	1	0	D = A + 1	Increment A
1	1	0	1	D = A - 1	Decrement A
1	1	1	1	D = A	Transfer A (Both Inc. & Dec.)

All the above basic arithmetic operations can be implemented through a unified composite arithmetic circuit that implements the logic of the adder-subtractor, incrementer, and decrementer in one combinational logic unit. A single composite arithmetic circuit unit will perform all such operations on a single bit and n circuits will be connected in series for operations on n-bit register inputs.

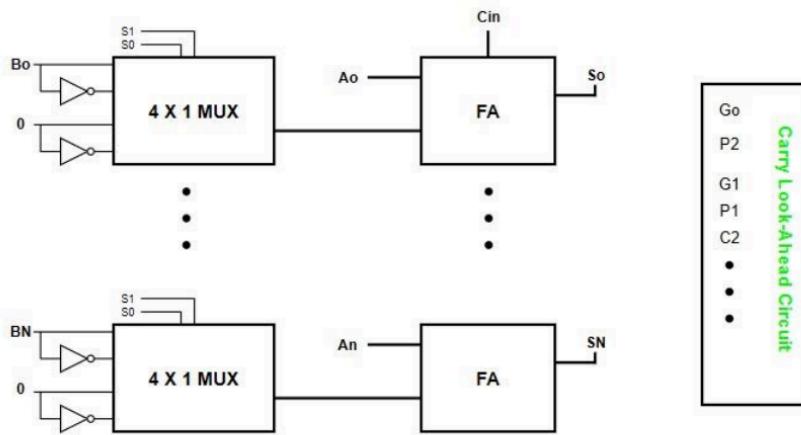


Figure 8-Arithmetic Circuit

2.4.2 Logic Microoperations

The logic unit contains eight gates instead of the previous four to increase the number of logic microoperations that can be performed within one clock cycle. Fig. 9 below showcases the logic unit. As shown, pins A and pin B connect separately to NOT gates. This means if the value at pin B needs to be inverted, it does not have to be transferred through the arithmetic circuit first to pin A that can be complemented directly, which is another improvement as compared to the Basic Computer. The logic unit uses an 8x1 MUX with 3 selection inputs to implement the circuit.

The table below summarizes the logical operations and their Boolean equivalents.

S₂	S₁	S₀	Output	Microoperation
0	0	0	$Y = A \wedge B$	AND
0	0	1	$Y = A \vee B$	OR
0	1	0	$Y = A \oplus B = (A \wedge B') \vee (A' \wedge B)$	XOR
0	1	1	$Y = (A \wedge B)' = A' \vee B'$	NAND
1	0	0	$Y = (A \vee B)' = A' \wedge B'$	NOR
1	0	1	$Y = (A \oplus B)' = (A \wedge B) \vee (A' \wedge B')$	XNOR
1	1	0	$Y = A'$	NOT
1	1	1	$Y = B'$	NOT

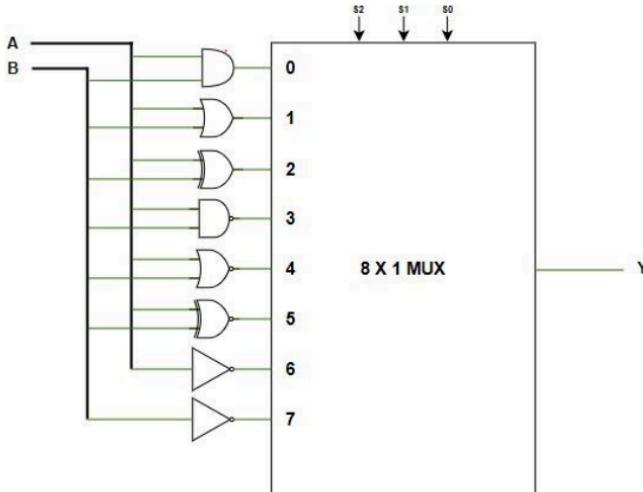


Figure 9-Logic Unit

2.4.3 Shift Microoperations



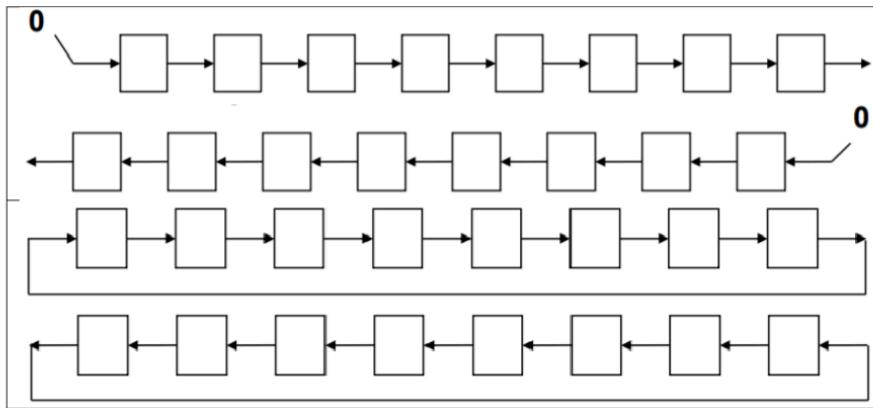
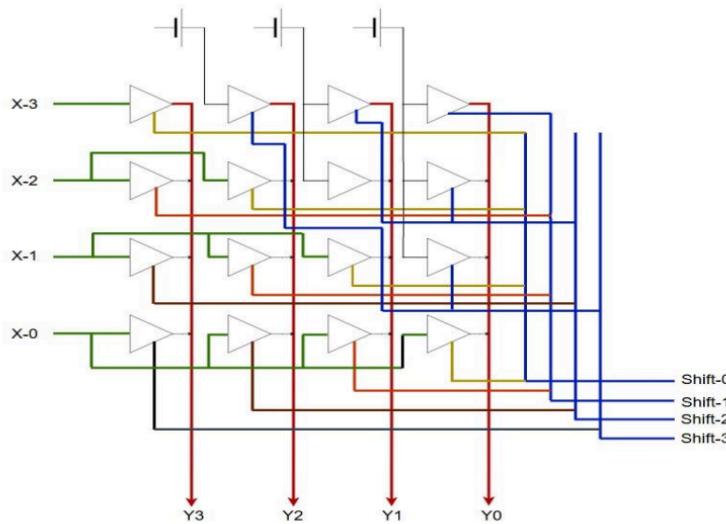


Figure 10-Logical shift right, Logical shift left, circular shift right, circular shift left (in order from top to bottom)

Fig. 10 summarizes the main shift operations that will be performed by the shift circuits of the ALU. The logical shift operations will append a 0 binary bit at the right-end (left shift). Unlike the Basic Computer, the B22Core processor utilizes the concept of barrel-shifter circuits, as shown below. The main advantage of this design selection is that the given circuit can perform up to three shifts in both left and right directions, and the circuit can be easily modified so that both circular and logical shifts can be implemented. The only major disadvantage that must be noted is that the barrel shifter circuit utilizes excessive hardwiring and thus is costly to implement practically. By implementing this logic, multiple shifts can be implemented under just one clock cycle. To select the number of shifts that will be performed on the operand, a 4 by 2 decoder will be connected with two select input lines.

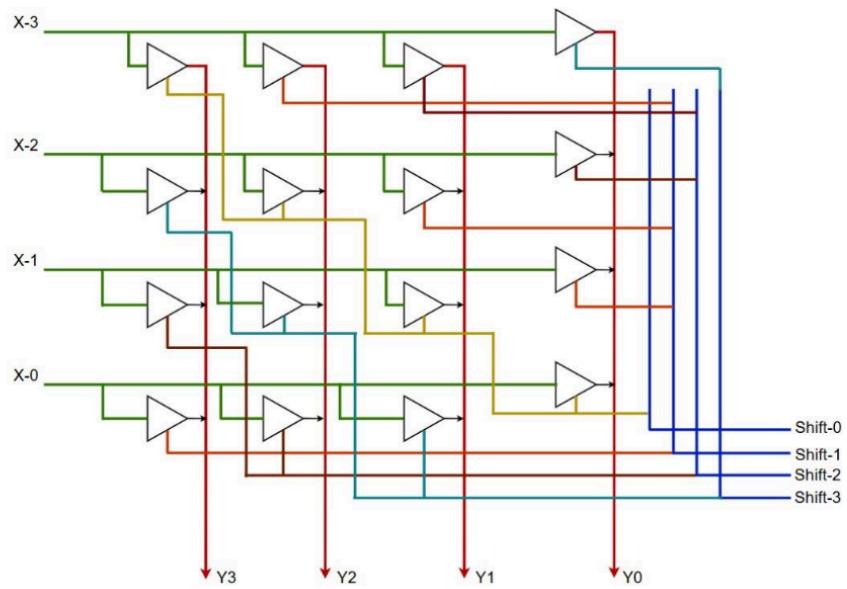

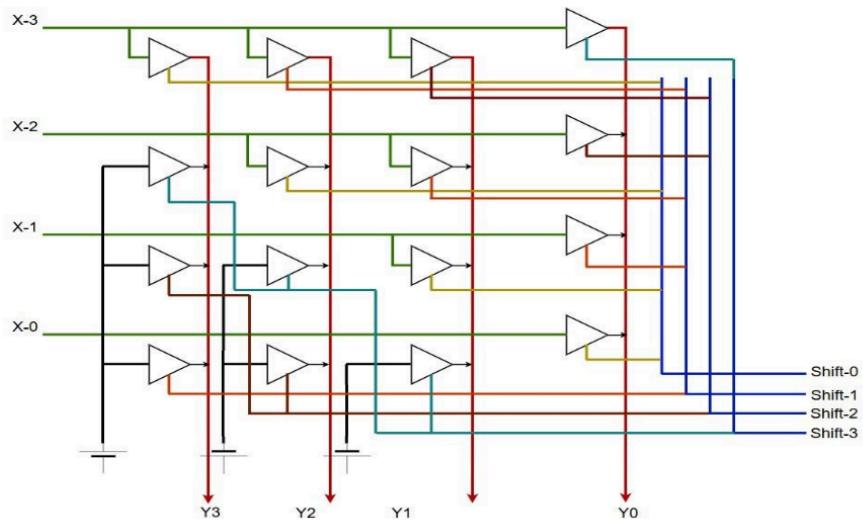

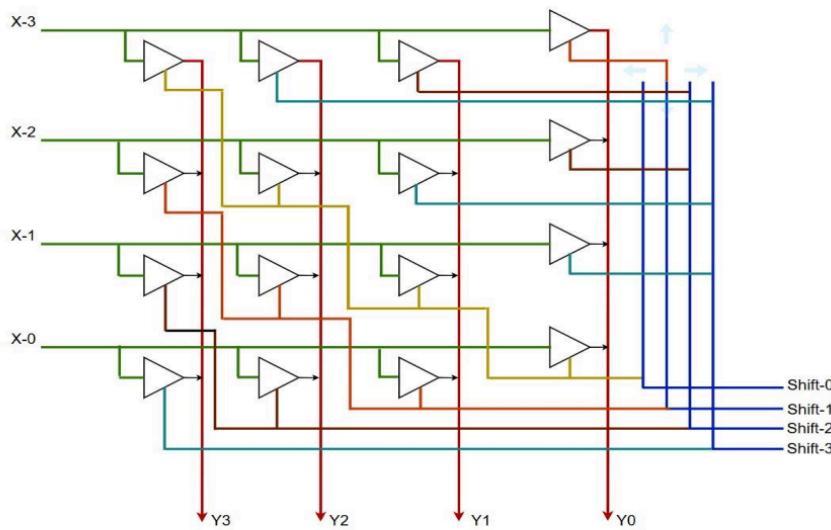


Figure 11-Logical shift left, Logical shift right, circular shift left, circular shift right (in order from top to bottom)

2.4.4 Miscellaneous Circuit Units for New Microoperations

In this section, some combinational circuits have been included in order to increase the functionality of B22Core processor, namely the comparator, gray to binary code converter and binary to gray code converter.

The circuit on the left hand side in Fig. 12 presents the gray code to binary converter whereas the one on the right specifies binary to gray code converter. The diagrams display their respective structures on a 4-bit input, but the same generalized pattern will follow from an n -bit register input in the ALU.

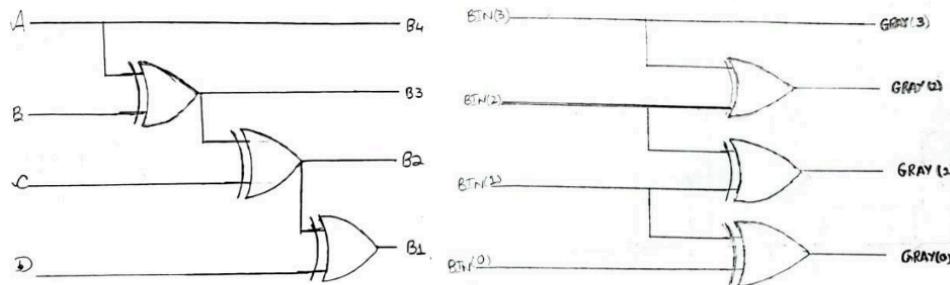


Figure 12-Gray-to-Binary (left) and Binary-to-Gray (right)

Lastly, Fig. 13 showcases the circuit of the comparator circuit. Once again, the input is only for a 4-bit register but the same pattern in logic can be enlarged to fit any n-bit register input application and thus is included as the final piece in the ALU of B22Core processor.

Comparator utilizes the use of as many XNOR gates as the number of input bits, which outputs 1 only if the two bits are equal. All the inputs are fed into a single AND gate which outputs 1 if and only if all the corresponding bits in the A and B inputs are the same.

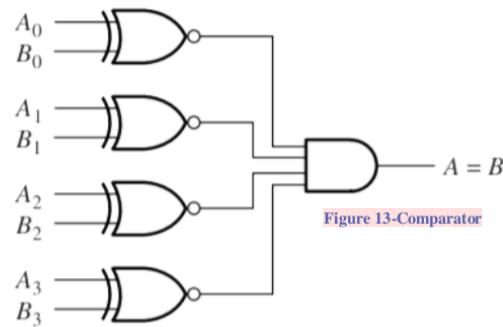


Figure 13-Comparator

2.4.5 Complete ALU Design

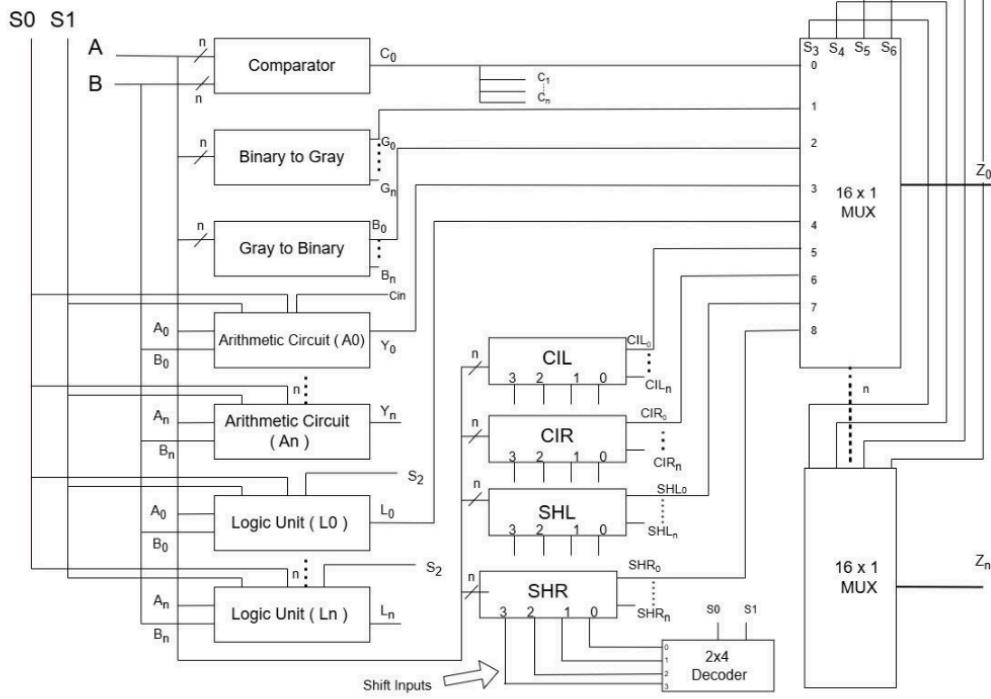


Figure 14-Complete ALU

S ₆	S ₅	S ₄	S ₃	S ₂	S ₁	S ₀	CIN	Operation	Function
0	0	0	0	x	x	x	x	A == B	Equality check using comparator
0	0	0	1	x	x	x	x	BIN \rightarrow GRAY	Conversion from binary to gray
0	0	1	0	x	x	x	x	GRAY \rightarrow BIN	Conversion from gray to binary
0	0	1	1	x	0	0	0	A + B	Addition
0	0	1	1	x	0	0	1	A + B + 1	Addition with carry
0	0	1	1	x	0	1	0	A + B'	Subtraction with borrow
0	0	1	1	x	0	1	1	A + B' + 1	Subtraction
0	0	1	1	x	1	0	0	A	Transfer
0	0	1	1	x	1	0	1	A + 1	Increment
0	0	1	1	x	1	1	0	A - 1	Decrement
0	0	1	1	x	1	1	1	A	Transfer
0	1	0	0	0	0	0	x	A \wedge B	AND
0	1	0	0	0	0	1	x	A \vee B	OR
0	1	0	0	0	1	0	x	A \oplus B	XOR
0	1	0	0	0	1	1	x	(A \wedge B)'	NAND
0	1	0	0	1	0	0	x	(A \vee B)'	NOR
0	1	0	0	1	0	1	x	(A \oplus B)'	XNOR
0	1	0	0	1	1	0	x	A'	COMPLEMENT A
0	1	0	0	1	1	1	x	B'	COMPLEMENT B
0	1	0	1	x	0	0	x	CIL 0	Circular shift left 0 times
0	1	0	1	x	0	1	x	CIL 1	Circular shift left 1 times
0	1	0	1	x	1	0	x	CIL 2	Circular shift left 2 times
0	1	0	1	x	1	1	x	CIL 3	Circular shift left 3 times
0	1	1	0	x	0	0	x	CIR 0	Circular shift right 0 times
0	1	1	0	x	0	1	x	CIR 1	Circular shift right 1 times
0	1	1	0	x	1	0	x	CIR 2	Circular shift right 2 times
0	1	1	0	x	1	1	x	CIR 3	Circular shift right 3 times
0	1	1	1	x	0	0	x	SHL 0	Logical shift left 0 times
0	1	1	1	x	0	1	x	SHL 1	Logical shift left 1 times
0	1	1	1	x	1	0	x	SHL 2	Logical shift left 2 times
0	1	1	1	x	1	1	x	SHL 3	Logical shift left 3 times
1	0	0	0	x	0	0	x	SHR 0	Logical shift right 0 times
1	0	0	0	x	0	1	x	SHR 1	Logical shift right 1 times
1	0	0	0	x	1	0	x	SHR 2	Logical shift right 2 times
1	0	0	0	x	1	1	x	SHR 3	Logical shift right 3 times

The above ALU designed specifically for the B22Core processor can perform arithmetic, logic, shift, comparison, and conversion operations on the inputs fed into the circuit. The corresponding truth table of the ALU succinctly captures the overall working of the circuit.

It must be noted that the output of the comparator is an n-bit output of all 1's or 0's depending on whether the two n-bit inputs are equal or not respectively. It must be noted that the nth bit output

of the individual circuits is inputted into the n^{th} 16 by 1 multiplexer. In addition, the barrel shifter circuits are connected to a 2 by 4 decoder that determines the number of shifts that will be performed on the n-bits of the register A.

Furthermore, the 16 by 1 MUX receives 9 inputs, and therefore the remaining 7 input pins are idle and unused, and thus not included in the truth table either for clarity.

2.5 Register Selection and Main Memory Organization

As already mentioned, the inclusion of a main memory for the storage of data and instructions is a necessity to correctly implement the von Neumann architecture. Main memory forms the backbone of all memory-reference instructions. It contains a unidirectional address bus for accessing specific words as indexed by the control unit whilst also incorporating a bidirectional data bus for reading and writing operations; in addition, ‘Read’ and ‘Write’ enable pins connect with the memory to specify the particular operation being performed by the control unit at given time.

The main memory comprises of 24-bit words, where bits 0 to 17 are used to store the operand or address.

Some other noteworthy features of the main memory are listed below:

- Memory contains $2^{18} = 262144$ unique storage cells of length 24 each.
- The address and data bus are 18- and 24-bits wide respectively.
- The Memory Address Register (i.e. AR) specifies the particular address in memory.
A write operation can be represented in RTL as $M[AR] \leftarrow B$ and read operation can be written as $B \leftarrow M[AR]$ where B is any arbitrary register in both cases.

2.5.1 Register Organization

The below table summarizes the processor registers that will be used to delegate certain roles to each register to form a common integrator in the next section which will be run and managed by the control unit to execute the Instruction Set Architecture (ISA).

Name of Register	Size (bits)	Function
Data Register (DR)	24	Holds the operand from memory which can be fed directly into the ALU for arithmetic and logic operations with the accumulator.
(Memory) Address Register (AR)	18	Stores the memory location where some data is to be written or stored usually after performing some memory-reference instruction.
Accumulator (AC)	24	Part of ALU; used to store intermediate arithmetic and logic operation results. The accumulator also connects to an E flip-flop called the Extended AC in case of any overflow conditions or for implementing shift operations in the
Program Counter (PC)	18	Points to the next address in memory storing the next instruction to be executed; increments by 1 sequentially

		at the start of every fetch-decode-execute cycle.
Temporary Register (TC)	24	Stores any data for short-term. Acts as an extra storage unit when needed. Useful for instructions such as exchange (EXC).
Instruction Register (IC)	24	Stores the instruction code of the instruction format.
Input Register (INPR)	16	Holds input character received from the input device; only the 16 least significant bits are connected to the bus; its contents are transferred to accumulator.
Output Register (OUTR)	16	Holds output character received from the accumulator and transfers it to the output device interface, and is not connected to any other register.

Some key points to note include:

- Each register has load (LD), increment (INC), clear (CLR) and clock (CLK) pins. Clock is fed into the registers from the Sequencer Counter (SC) and the former three pins are managed by the control logic of the control unit.
- The accumulator's ALU takes input from the outputs of DR, INPR, and AC itself.
- The INPR and OUTR both have 16-bits so that the B22Core processor is compatible with the Unicode Standard and can store 16-bit defined characters whereas the Basic Computer was only compatible with ASCII Character Set.

2.6 Instruction Format

The format of the memory word can describe three different categories of instructions, namely:

- Memory-Reference Instructions-operate by manipulating the data and instructions in the main memory for various applications.
- Register-Reference Instructions-operate directly on the registers defined within the processor without the need of specifying an operand in the main memory.
- Input-Output Instructions-deal with external input and output operations which may be required during the execution of any program.

Type of Instruction	Description	Format										
Memory-Reference Instruction	Uses one bit to specify the addressing mode I. I is equal to 0 for direct address and to 1 for indirect address. (Op-code = 00000-11110)	<table border="1"> <tr> <td>23</td> <td>22</td> <td>18</td> <td>17</td> <td>0</td> </tr> <tr> <td>I</td> <td>Opcode</td> <td colspan="2">Address</td> <td></td> </tr> </table>	23	22	18	17	0	I	Opcode	Address		
23	22	18	17	0								
I	Opcode	Address										
Register-Reference Instruction	The addressing mode bit I is always 0. (Op-code = 11111, I = 0)	<table border="1"> <tr> <td>23</td> <td>22</td> <td>18</td> <td>17</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>1</td> <td>Register operation</td> </tr> </table>	23	22	18	17	0	0	1	1	1	Register operation
23	22	18	17	0								
0	1	1	1	Register operation								

Input/Output- Instruction	The addressing mode bit is always 1. (Op-code = 1111, I = 1)	<table border="1"> <tr> <td>23</td><td>22</td><td>18</td><td>17</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>1</td><td>1</td><td>I/O operation</td></tr> </table>	23	22	18	17	0	1	1	1	1	I/O operation
23	22	18	17	0								
1	1	1	1	I/O operation								

The B22Core processor accomplishes indirect and direct addressing by dedicating the 23rd bit dedicated to specifying the addressing modes (i.e. indirect and direct). In the case of direct addressing, the operand stored in memory will be accessed and transferred directly for the execution phase; in contrast, indirect addressing mode entails the use of an extra referencing step from memory to retrieve the effective address (i.e. EA) of the operand.

Furthermore, 5 bits are dedicated to specify the operation code (here onward referred to as opcode).

2.7 The Common Integrator

This section briefly details the overall structural organization of the processor registers defined in the previous sections. As shown, the registers connect to a 24-bit common bus and the loading and reading to and from the registers is performed by the three select inputs S₂, S₁, and S₀.

Some notable features of the common integrator include how the AC does not connect directly with the bus for any write operations and instead is fed inputs by the ALU which received inputs from the outputs of AC, DR, and INPR. The OUTR does not connect with the common bus for any reading purposes as contents are shown directly on the external output interface; by the same token, INPR does not connect to the bus for either reading or writing since the input is fed into the register externally and its value is directly passed to the ALU. The implementation of the common bus saves circuitry that would otherwise have been used to connect individual registers in direct connections with each other.

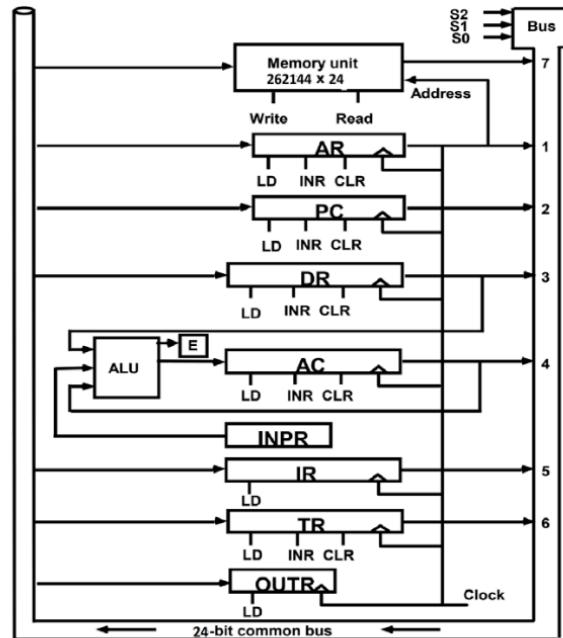


Figure 15-Common Integrator

3. Definition & Implementation of the Instruction Set

The instructions implemented by the B22Core processor are outlined in the table below. For convenience, the opcode instructions have been digitally represented using octal number system as the base 8 system is divisible by the size of B22Core processor's instruction size of 24 bits.

Symbol	Octal Code		Description
	I = 0	I = 1	
Memory-Reference Instructions			
ADD	00xxxxxx	40xxxxxx	Add content of memory to accumulator.
SUB	01xxxxxx	41xxxxxx	Subtract content of memory from accumulator.
BUN	02xxxxxx	42xxxxxx	Jumps/branches execution to a specified point.
BSA	03xxxxxx	43xxxxxx	Branch and save return Address.
LDA	04xxxxxx	44xxxxxx	Load content into accumulator from memory.
STA	05xxxxxx	45xxxxxx	Store content into memory from accumulator.
AND	06xxxxxx	46xxxxxx	AND memory with accumulator.
OR	07xxxxxx	47xxxxxx	OR memory with accumulator.
XOR	10xxxxxx	50xxxxxx	XOR memory with accumulator.
NAND	11xxxxxx	51xxxxxx	NAND memory with accumulator.
NOR	12xxxxxx	52xxxxxx	NOR memory with accumulator.
XNOR	13xxxxxx	53xxxxxx	XNOR memory with accumulator.
NOT	14xxxxxx	54xxxxxx	NOT memory with accumulator.
INC	15xxxxxx	55xxxxxx	Increment contents of accumulator.
DEC	16xxxxxx	56xxxxxx	Decrement contents of accumulator.
GTB	17xxxxxx	57xxxxxx	Convert gray to binary code.
BTG	20xxxxxx	60xxxxxx	Convert binary to gray code.
EQL	21xxxxxx	61xxxxxx	Check equality of content between AC and memory word.
EXC	22xxxxxx	62xxxxxx	Exchange the contents of AC and memory.
TCA	23xxxxxx	63xxxxxx	Twos complement of the AC.
SHL	24xxxxxx	64xxxxxx	Logical shift left.
SHR	25xxxxxx	65xxxxxx	Logical shift right.
CIL	26xxxxxx	66xxxxxx	Circular shift left.
CIR	27xxxxxx	67xxxxxx	Circular shift right.
ISZ	30xxxxxx	70xxxxxx	Increment and skip if zero.
Register-Reference Instructions			
CLA	37000001		Clear accumulator.
CLE	37000002		Clear extended accumulator.
CMA	37000003		Complement accumulator.
CME	37000004		Complement extended AC flip-flop.
CIR	37000005		Circular shift right AC and E.
CIL	37000006		Circular shift left AC and E.
INC	37000007		Increment AC.
SPA	37000010		Skip next instruction if AC is positive.

SNA	37000011	Skip next instruction if AC is negative.
SZA	37000012	Skip next instruction if AC is zero.
SZE	37000013	Skip next instruction if E is zero.
HLT	37000014	Halt computer execution.
Input/Output Reference Instructions		
INP	77000001	Input data to register.
OUT	77000002	Output data to register.
SKI	77000003	Skip on input flag.
SKO	77000004	Skip on output flag.
ION	77000005	Interrupt on.
IOF	77000006	Interrupt off.

The instruction set as outlined above is functionally complete as it includes all the categories of instructions used by assembly language programmers to execute their programs, namely: the arithmetic, shift and logic instructions; data transfer instructions; program sequencing control and status instructions; input and output instructions. Since the usage of subroutines is common across all applications of computer processing, it was imperative to provide this functionality hardwired within the machine instruction set of the B22Core processor to facilitate subroutine entry to and from the main program.

3.1 The Control Unit

Control unit fetches code for instructions from microprograms and directs other units and models by providing control and timing signals. The function of the Control unit is as follows:

- Controls sequential instruction execution
- Interprets instructions
- Regulates and controls processor timing
- Sends and receives control signals from other computer devices
- Handles multiple tasks, such as fetching, decoding, execution handling and storing results.

The control unit comprises of two decoders (5-32) and (4-16), one four-bit sequence counter and other logical circuits. The 5-32 decoder takes five bits from the instruction register and decodes it to acquire the desired set of microoperations. The five bits are used to produce the 32 instructions where each instruction has its own micro-operation. The control unit also provides the CPU timing signals to sequentially execute the instructions to be performed. The binary value of the 4-bit sequence counter is fed into the decoder, and together the two units function similar to a ring counter, in which a bit value of 1 is cycled through the timing states one at a time.

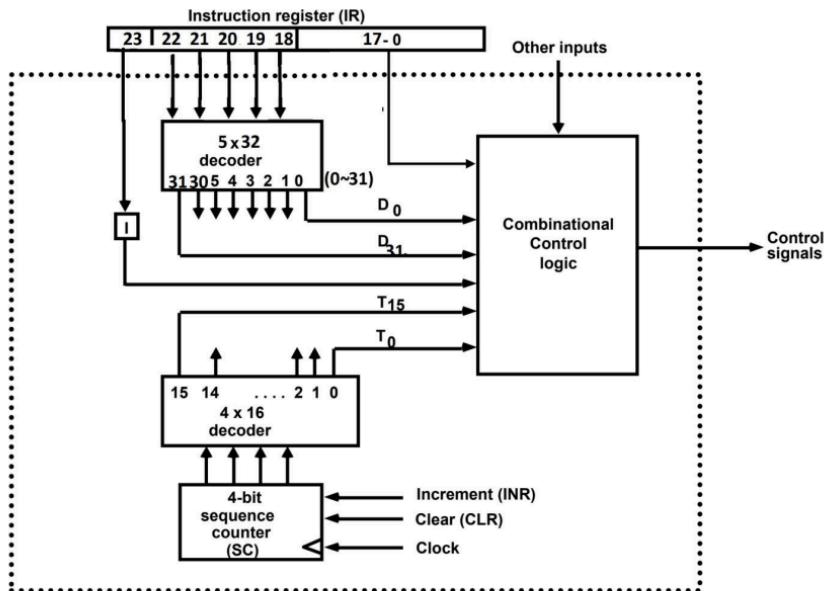


Figure 16-Control Unit

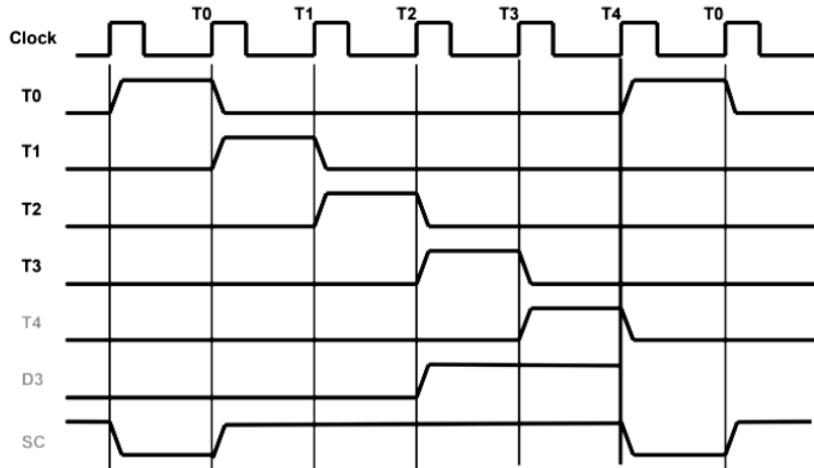


Figure 17-Sequencer and Decoder Combination Waveform


SC_3	SC_2	SC_1	SC_0	T_0	T_1	T_2	T_3	T_4	T_5	T_6	T_7	T_8	T_9	T_{10}	T_{11}	T_{12}	T_{13}	T_{14}	T_{15}
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	
0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	
0	1	0	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	
0	1	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	
0	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	
1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	
1	0	0	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	
1	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	
1	0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	
1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	

Figure 18-Sequencer and Decoder Combination Truth Table

Four-bit sequence counter generates the output which will be decoded in the decoder to generate the control signals from T_0 to T_{15} . After every instruction the sequence counter is reset to zero to again perform the fetch and decode cycle. Initially the sequence counter is zero so the decoder will generate the timing signal T_0 . The timing signal T_0 will select the PC from the 24-bit common bus and AR from the logic circuit. This control signal is received by the integrated circuit and transfers the address from PC to AR during the clock transition associated with timing signal T_0 . At timing signal T_1 , AR will be selected and the instruction read from memory will be placed in the instruction register.

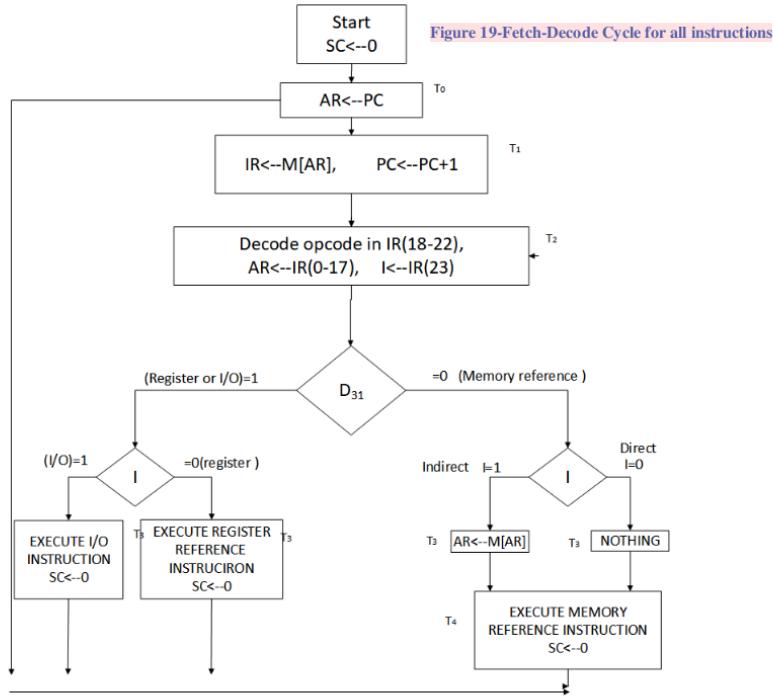3.3 Fetch-Decode Cycle

The below flowchart summarizes the fetch and decode cycles that occurs at the start of every timing state. Following this cycle, the specific execute sequences microoperations for each instruction will be executed, given in the complete computer description.



3.2 Input/Output and Interrupt Handling

Computer contains output flag and input flag to inform the processor what the user wants to input data or output data. The processor continuously checks that any of the flag are active (flag=1) or not (flag=0). It is one of the reasons that the cursor blinks and when user strikes a key, or input data the input flag (FGI=1) is active and processor store data in input register and then to accumulator. similarly, when the user wants to output data, the output flag (FGO=1) is active and the data from accumulator is copied to output register. In basic computer it has an interrupt enable function (IEN). The interrupt helps in a way that when interrupt is active, it stops all background processing and performs the task. As in displayed in figure below which show how a computer works combining IEN, FGO, FGI. First the processor checks that if the interrupt is

active or not. If not, it fetches and decodes instructions. If (IEN=1) it checks that whether the output flag is active or input flag and enables Interrupt r flip-flop. All operations are paused, and the return address is stored. In location 0 for example and the instruction stored in the location '1' is performed first, which may contain the input/output subroutine. At the end of subroutine is the indirect BUN which resumes the main program executions.

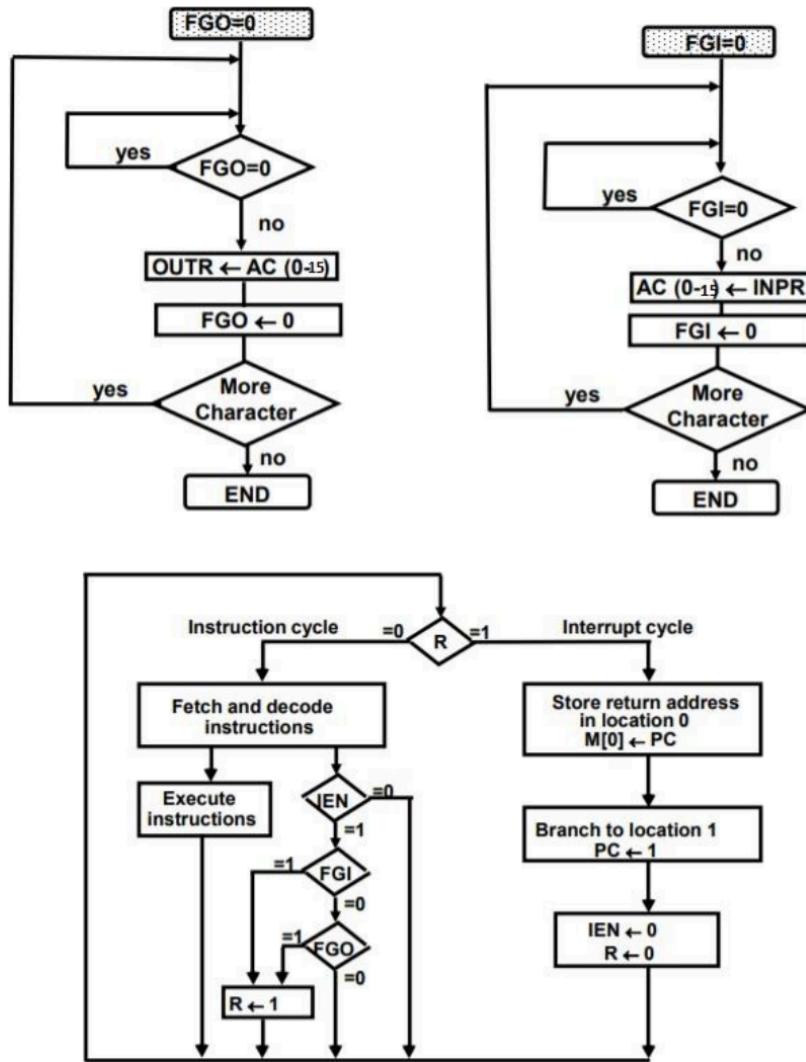


Figure 20-Input/Output Handling Flowcharts

4. Complete Computer Description

Fetch-Decode Cycle		
Fetch		
R'T ₀ :		AR ← PC
R'T ₁ :		IR ← M[AR], PC ← PC + 1
Decode		
R'T ₂ :	D ₀ , ..., D ₃₁	← Decode IR(18~22), AR ← IR(0~17), I ← IR(23)
Indirect Addressing		
D ₇ 'IT ₃ :		AR ← M[AR]
Interrupt		
T ₀ 'T ₁ 'T ₂ '(IEN)(FGI+FGO)		R ← 1
RT ₀		AR ← 0, TR ← PC
RT ₁		M[AR] ← TR, PC ← 0
RT ₂		PC ← PC + 1, IEN ← 0, SC ← 0
Execution Cycles		
Memory-Reference		
ADD	D ₀ T ₄	DR ← M[AR]
	D ₀ T ₅	AC ← AC + DR, E ← C _{out} , SC ← 0
SUB	D ₁ T ₄	AC ← TR, M[AR] ← DR
	D ₁ T ₅	DR ← AC
	D ₁ T ₆	AC ← AC'
	D ₁ T ₇	AC ← AC + 1
	D ₁ T ₈	AC ← AC + TR, E ← C _{out} , SC ← 0
BUN	D ₂ T ₄	AR ← PC, SC ← 0
BSA	D ₃ T ₄	M[AR] ← PC, AR ← AR + 1
	D ₃ T ₅	PC ← AR, SC ← 0
LDA	D ₄ T ₄	M[AR] ← PC, SC ← 0
STA	D ₅ T ₄	DR ← M[AR]
	D ₅ T ₅	AC ← DR, SC ← 0
AND	D ₆ T ₄	DR ← M[AR]
	D ₆ T ₅	AC ← AC ∧ DR, SC ← 0
OR	D ₇ T ₄	DR ← M[AR]
	D ₇ T ₅	AC ← AC ∨ DR, SC ← 0
XOR	D ₈ T ₄	DR ← M[AR]
	D ₈ T ₅	AC ← AC ⊕ DR, SC ← 0
NAND	D ₉ T ₄	DR ← M[AR]
	D ₉ T ₅	AC ← AC (nand) DR, SC ← 0
NOR	D ₁₀ T ₄	DR ← M[AR]
	D ₁₀ T ₅	AC ← AC (nor) DR, SC ← 0
XNOR	D ₁₁ T ₄	DR ← M[AR]

	D ₁₁ T ₃	AC ← AC (xnor) DR, SC ← 0
NOT	D ₁₂ T ₄	DR ← M[AR]
	D ₁₂ T ₅	AC ← DR
	D ₁₂ T ₆	AC ← AC', SC ← 0
INC	D ₁₃ T ₄	DR ← M[AR]
	D ₁₃ T ₅	AC ← DR
	D ₁₃ T ₆	AC ← AC + 1, SC ← 0
DEC	D ₁₄ T ₄	DR ← M[AR]
	D ₁₄ T ₅	AC ← DR
	D ₁₄ T ₆	AC ← AC - 1, SC ← 0
GTB	D ₁₅ T ₄	DR ← M[AR]
	D ₁₅ T ₅	AC ← DR
	D ₁₅ T ₆	AC ← gtb AC, SC ← 0
BTG	D ₁₆ T ₄	DR ← M[AR]
	D ₁₆ T ₅	AC ← DR
	D ₁₆ T ₆	AC ← btg AC, SC ← 0
EQL	D ₁₇ T ₄	DR ← M[AR]
	D ₁₇ T ₅	AC ← AC == DR, SC ← 0
EXC	D ₁₈ T ₄	DR ← M[AR]
	D ₁₈ T ₅	M[AR] ← AC
	D ₁₈ T ₆	AC ← DR, SC ← 0
TCA	D ₁₉ T ₄	DR ← M[AR]
	D ₁₉ T ₅	AC ← DR
	D ₁₉ T ₆	AC ← AC'
	D ₁₉ T ₇	AC ← AC + 1, SC ← 0
SHL	D ₂₀ T ₄	DR ← M[AR]
	D ₂₀ T ₅	AC ← DR
	D ₂₀ T ₆	AC ← shl AC, SC ← 0
SHR	D ₂₁ T ₄	DR ← M[AR]
	D ₂₁ T ₅	AC ← DR
	D ₂₁ T ₆	AC ← shr AC, SC ← 0
CIL	D ₂₂ T ₄	DR ← M[AR]
	D ₂₂ T ₅	AC ← DR
	D ₂₂ T ₆	AC ← cil AC, SC ← 0
CIR	D ₂₃ T ₄	DR ← M[AR]
	D ₂₃ T ₅	AC ← DR
	D ₂₃ T ₆	AC ← cir AC, SC ← 0
ISZ	D ₂₄ T ₄	DR ← M[AR]
	D ₂₄ T ₅	DR ← DR + 1
	D ₂₄ T ₆	M[AR] ← DR, if (DR=0) then (PC ← PC + 1), SC ← 0

Execution Cycles		
Register-Reference ($r = D_3iIT_3$) Bi where i is the decimal equivalent of the octal code		
CLA	rB ₁	AC $\leftarrow 0$
CLE	rB ₂	E $\leftarrow 0$
CMA	rB ₃	AC $\leftarrow AC'$
CME	rB ₄	E $\leftarrow E'$
CIR	rB ₅	AC $\leftarrow shr AC, AC(23) \leftarrow E, E \leftarrow AC(0)$
CIL	rB ₆	AC $\leftarrow shl AC, AC(0) \leftarrow E, E \leftarrow AC(23)$
INC	rB ₇	AC $\leftarrow AC + 1$
SPA	rB ₈	If (AC(23) = 0) then (PC $\leftarrow PC + 1$)
SNA	rB ₉	If (AC(23) = 1) then (PC $\leftarrow PC + 1$)
SZA	rB ₁₀	If (AC = 0) then (PC $\leftarrow PC + 1$)
SZE	rB ₁₁	If (E = 0) then (PC $\leftarrow PC + 1$)
END	rB ₁₂	S $\leftarrow 0$


Execution Cycles		
Input/Output-Reference ($p = D_3iT_3$) Bi where i is the decimal equivalent of the octal code		
INP	pB ₁	AC(0-15) $\leftarrow INPR, FGI \leftarrow 0$
OUT	pB ₂	OUTR $\leftarrow AC(0-15), FGO \leftarrow 0$
SKI	pB ₃	If (FGI=1) then (PC $\leftarrow PC + 1$)
SKO	pB ₄	If (FGO=1) then (PC $\leftarrow PC + 1$)
ION	pB ₅	IEN $\leftarrow 1$
IOF	pB ₆	IEN $\leftarrow 0$

5. C++ Simulator

In order to facilitate a visual implementation of the theoretically constructed B22Core processor's organization, an original simulator was programmed by members of our team to emulate the basic computer in order to give an idea of how the B22Core processor would be implemented. The simulator was programmed in C++ and can be downloaded with this project. A separate handbook detailing the working of the simulator can also be found which contains all the required information to operate the simulator.


Appendix

A. Decoder

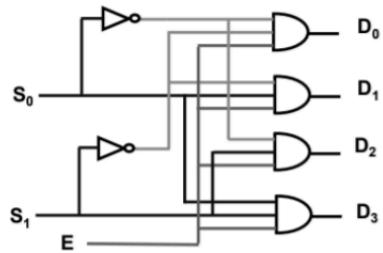


E	S ₁	S ₀	D ₀	D ₁	D ₂	D ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	d	d	0	0	0	0


B. Three State Gate

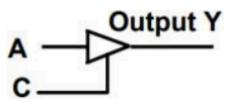


C	A	Y
1	0	0
1	1	1
0	0	Disabled (High Impedance)

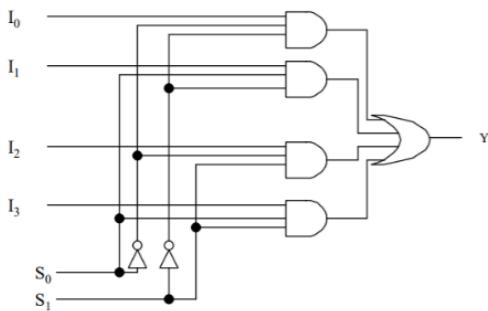C. Multiplexer

S₁	S₀	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

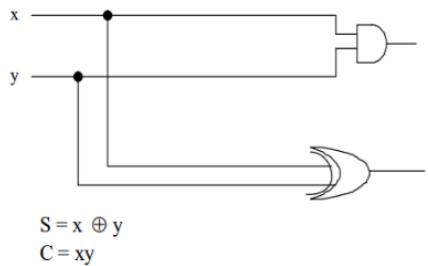D. Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

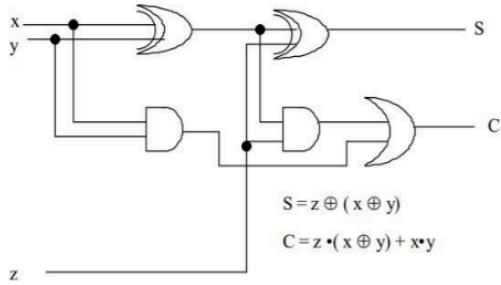E. Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Bibliography

- [1] Thomas L.Floyd, Digital Fundamentals, 11th Edition, Pearson, July 2014,
ISBN: 9780132737968.
- [2] Microsoft Visio, 2013.
- [3] Paint, 2013.
- [4] Morris Mano, Computer System Architecture, 3rd Edition,
ISBN: 9788120308558.
- [5] Albert P. Malvino & Jerald A. Brown, Digital Computer Electronics, 3rd Edition,
McGraw-Hill, 1993,
ISBN: 9780028005942.
- [6] Mohamed Rafiquzzaman, Fundamentals of Digital Logic and Microcomputer Design,
5th Edition, Wiley-Interscience, 2005, ISBN: 9780471727842.
- [7] David Harris & Sarah L. Harris, Digital Design and Computer Architecture, 2021,
ISBN: 9780128200643
- [8] William Stallings, Computer Organization and Architecture: Designing for
performance, 11th Edition, ISBN: 9780134997193.
- [9] Douglas Comer, Essentials of Computer Architecture, 2004,
ISBN: 9780367573959.
- [10] John P. Shen & Mikko H. Lipasti, Modern Processor Design, 2003,
ISBN: 9780070570641.

Assignment

ORIGINALITY REPORT



PRIMARY SOURCES

1 Submitted to Higher Education Commission
Pakistan

Student Paper

Exclude quotes Off

Exclude matches Off

Exclude bibliography On

Assignment

GRADEMARK REPORT

FINAL GRADE

GENERAL COMMENTS

/0

PAGE 1

PAGE 2

PAGE 3

PAGE 4

PAGE 5

PAGE 6

PAGE 7

PAGE 8

PAGE 9

PAGE 10

PAGE 11

PAGE 12

PAGE 13

PAGE 14

PAGE 15

PAGE 16

PAGE 17

PAGE 18

PAGE 19

PAGE 20

PAGE 21

PAGE 22

PAGE 23

PAGE 24

PAGE 25

PAGE 26

PAGE 27

PAGE 28

PAGE 29

PAGE 30

PAGE 31

PAGE 32
